

MODEL QUESTION PAPER

DSE1

III Semester DIPLOMA Examination, August 2011 CIRCUIT THEORY

Time: 3 Hours

Max. Marks: 75

GROUP A : Answer any three questions.

- Q.1 Explain construction and working of RLC parallel resistance circuit.
- Q.2 Explain the construction details of RLC transient circuit.
- Q.3 Write the expression for delta to star conversion.
- Q.4 Derive the expression for measuring power and power factor in a three phase circuit by using two Watt meter for balanced load.
- Q.5 Explain node analysis method with example.

GROUP B : Answer any three questions.

- Q.6 Explain Resistance transient circuit.
- Q.7 What is the relationship between frequency and inductive reactance?
- Q.8 Derive current expression for RLC transient circuit. Also explain RL Decay transient.
- Q.9 Draw the vector diagram of pure inductor and pure capacitor circuit.
- Q.10 Derive the expression for energy stored in capacitor.

GROUP C: All Questions are Compulsory.

Q.11 Fill in the blanks

- (i) Capacitive reactance is _____ proportional to frequency.
- (ii) RMS Value = _____.
- (iii) The total power in 3 phase balanced load can be measured by _____.
- (iv) _____ is the property of conductor while opposes the flow of current through it.
- (v) Mesh analysis is using _____ law.

Q.12 Multiple choice question.

- (i) In which circuit voltage across each resistance is the same _____.
 - (a) Series circuit
 - (b) Parallel circuit
 - (c) Series- parallel circuit
 - (d) Parallel series circuit.
- (ii) KVL is used to solve _____.
 - (a) Mesh
 - (b) Loop
 - (c) Branch
 - (d) Power
- (iii) Watt is a unit for _____.
 - (a) Power
 - (b) Current
 - (c) Voltage
 - (d) Frequency

- (iv) Unit of electrical energy is _____
(a) Joules (b) Ohm
(c) Mho (d) Joules/sec
- (v) Electric energy = _____.
(a) Power \times Time (b) Current \times Time
(c) Voltage \times time (d) None of above

Q.13 True or false

- (i) Super position theorem is only applicable for determining power not voltage & current.
- (ii) Work done in electric circuit generates power.
- (iii) The maximum +ve(positive) or -ve(Negative) value of an alternating is called amplitude or peak value.
- (iv) Power = $V \times I$.
- (v) A 3 phase system can be set up a rotating magnetic field in stationary winding.
